


Alachua County NFARC Winkeyer Emulation

A LabNLunch Project!

August, 2024

Gordon Gibby KX4Z

Version 0.1

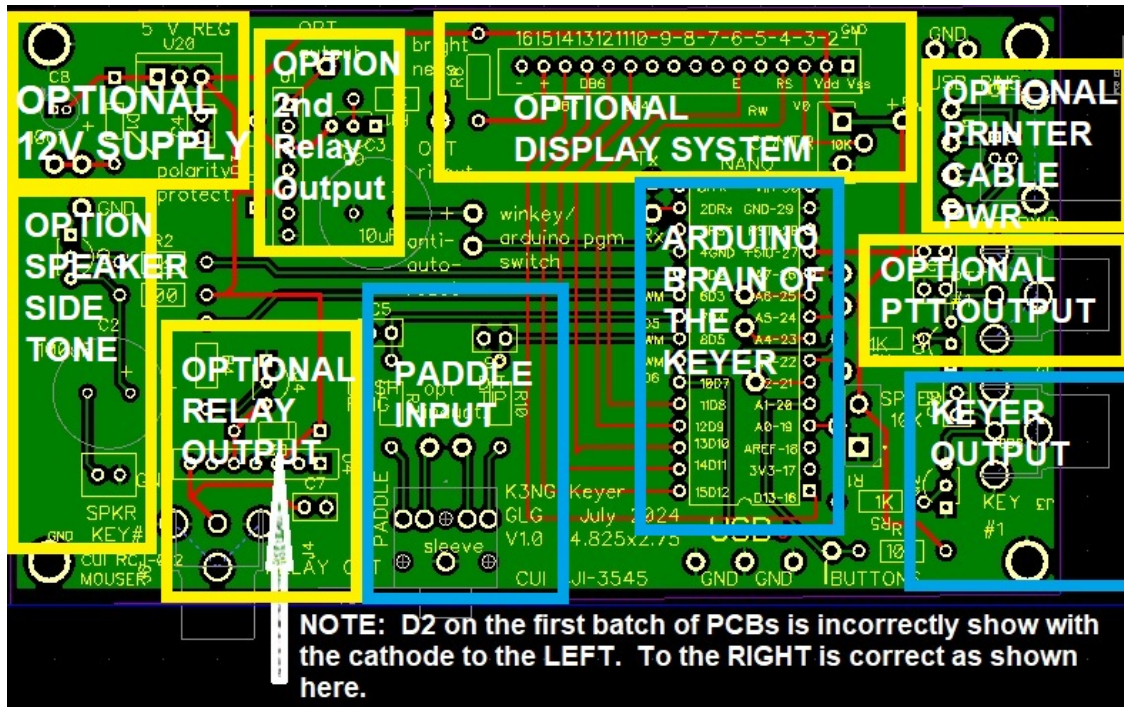


SECTIONS OF THE BOARD

CONTENTS

Section	Topic	Comments	Page
0	Illustrated sections of the board	Blue encased = required	2
1	Features and Specifications		5
2	Operating Instructions	Very useful instructions!	6
	BUILDING:		
3	Optional 12V Supply	If you are going to install this, do it first and test before adding the Arduino	8
4	Paddle Input	TRS 3.5mm "stereo" jack	10
5	Keyer Output #1	RCA Phono Plug Jack	11
6	Arduino Nano Microcontroller	The brains of the entire system	12
7	Optional Speaker Sidetone	Allows you to hear what you are sending	13
8	Optional Display	Allows you to see what you are sending	14
9	Optional PTT output	Very helpful in shortening needless VOX delays	15
10	Potentiometer Speed Control	One of the easiest ways to adjust speed	16
11	Buttons	Command and memory buttons	16
12	Optional Relay Output (Keyed Line)	Required for negative or high voltage keyed lines (e.g. Heathkit)	17
13	Programming Notes		18
14	Schematic	(incomplete)	19
15	Components Required		19
16	Approximate Costs		20

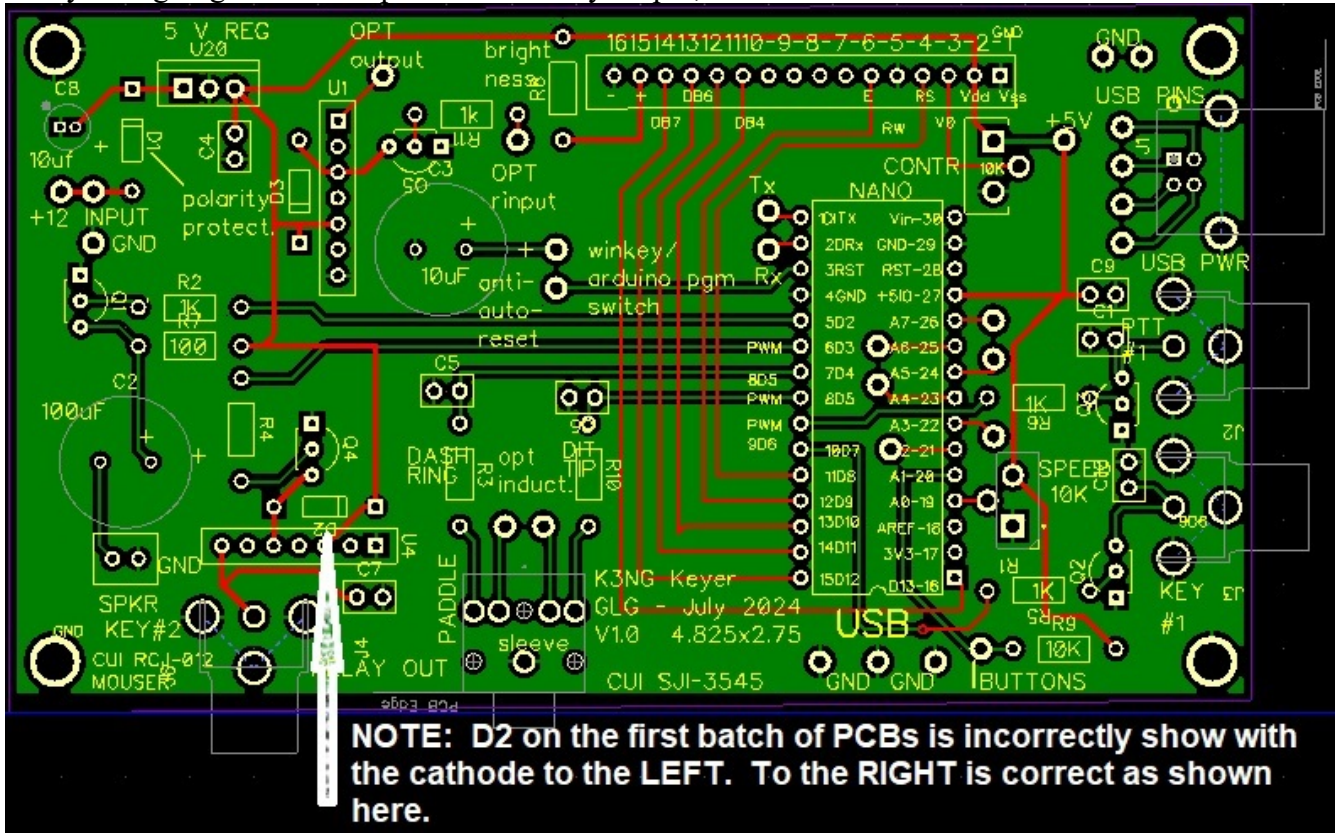If you're going to use the optional reed relay output, notice that the diode is mismarked backwards.



FEATURES AND SPECIFICATIONS

Stand-alone Electronic Keyer	Memory keyer	WINKEYER emulation
<ul style="list-style-type: none"> • Can be powered by either USB 5-volt source or 12-V source -- can be operated easily in the field with NO COMPUTER for POTA! • Simple TRS 3.5mm stereo paddle connections • Standard: Iambic A • Potentiometer easy speed adjust • 5-30 wpm base unit; can be expanded • Key line output open collector (2N3904) keys up to 10V, 20mA • PTT output open collector can key linear or transceiver with delays for relay actuation • Available reed-relay output for negative voltage, or high voltage (e.g. older vacuum tube transceiver) keying requirements • Available display shows word per minute setting and also shows all transmitted characters. • Speed can also be raised or lowered using command button and holding either dit or dash paddle • Does everything you need for a simple electronic keyer! 	<ul style="list-style-type: none"> • Typical memory keyer construction has 3 memories, but this can also be expanded. • Memory text can be set to automatically repeat if desired; simple setting using paddle and individual button (hold button, touch dit paddle) • Repeat on/off is individually set for each memory text ("canned text") • Delay between repeats is also adjustable (same delay for any repeated) • If available display is installed, memory text is also displayed during transmit. • Memories are programmed using the paddle; no keyboard required. • Memories are maintained in non-volatile memory between instances of use. 	<ul style="list-style-type: none"> • Provides Version 2.3 WINKEYER emulation • Works correctly with N3FJP • (Keying speed has been re-tuned <u>to be primary with the keyer</u>, not the computer for increased control.) • Standard 1200 baud WINKEYER emulation • Simply connect USB cable to the USB 2.0 Micro B jack on the Arduino Nano. • N3FJP provides for both canned text and direct keyboard to keyer sending as well (F12 key) • Will work with any logging system that keys using Winkeyer 2 protocol. • Does everything you need to have a winning Field Day effort!

OPERATION

NORMAL MODE

1. **STRAIGHT KEY MODE:** (rare) If you are holding the DASH arm pressed when you turn it on, it becomes a simple straight key (not a keyer) -- and the DOT arm is the Morse code straight key. Not sure when you would want this, but you can do it.
2. **SETTING KEYER SPEED:** When you normally turn it on, the Speed Potentiometer sets the KEYER speed. When you turn it, if there is a display, it will immediately start showing you your chosen speed.
3. **SENDING MEMORY TEXT:** If you press any of the MEMORY BUTTONS, it will start sending that memory canned text. It remembers them in non-volatile memory.
4. **REPEATING MEMORY TEXT:** If, while you press one of the MEMORY BUTTONS, you also press the DOT paddle, you have activated "repeat" and THAT memory will now repeat at the setting you assigned (see later). Repeating or not is unique to each memory. You have have whichever ones you want repeat.

COMMAND MODE

5. If you press the COMMAND button, you enter command mode. The screen will tell you that. I recommend a somewhat slower command speed so you don't make mistakes. But if you turn the potentiometer, you can change the speed of the command mode.
6. **EXITING COMMAND MODE:** If you press the COMMAND button again, or send X on the paddles, it will eXit command mode.
7. **USEFUL COMMAND MODE COMMANDS:** Other commands you can do while you are in COMMAND mode: (I selected what I thought were the most useful choices)

P1 <send the message> (fill the Memory #1)
P2 <send the message> (fill the Memory #2)
P3 <send the message> (fill the Memory #3)

*Press the COMMAND button to terminate entry of the programmable memory text.
It will then send you back the message so you can hear what you have stored.
Press COMMAND again to get out of command mode*

N -- causes the dot and dash paddles to swap sides. It is a "toggle" so you send N again to reverse back (remember, you swapped them, right?)
O -- cycles between three settings for the SIDETONE: ON, OFF, and PADDLE ONLY. It will show you on the screen

Y -- sets the time delay between memory repeats. 400 = 4 seconds, for example

T -- tune mode. This is very useful but also a bit confusing. Once you are in TUNE mode, you can hit COMMAND to exit, or press both paddles simultaneously. While in TUNE mode:

- Pressing the DASH arm starts a continuous transmit until you press it again
- Pressing the DOT arm acts like a Morse straight key-- it transmits as long as you hold it down.

NOTE: Exactly as you would want, the keyer does not key the transmitter while you are in command mode.


WINKEYER EMULATION

8. It also works with N3FJP in **Winkeyer emulation**. You plug a USB cable into the tiny connector right on the Arduino (Micro USB). A short connector comes with the Arduino. You can get longer ones. I suspect it will work perfectly with N1MM also. I haven't tested Log4OM yet.

9. **Commands that were left out:** There are zillion OTHER commands but each one takes a bit of memory and I am at 96% full so far so not much much more can be added..... It is an amazing keyer at this point. The USB-Winkeyer that I have was \$140, works GREAT, but does not have a display. So this is really really cool for far less \$\$\$\$

10. **Display:** It is always showing you what you are typing, right on the display. Inside N3FJP, for example, you can hit F12 and then use the keyboard of your computer to "type" Morse code -- and the keyer will send it for you! Whatever letters you type, it sends--and shows you. Since we did NOT add a keyboard to the keyer, it doesn't have its own keyboard. Not enough memory left. But pretty amazing what you can do with this!

13.8VDC Power Source Option

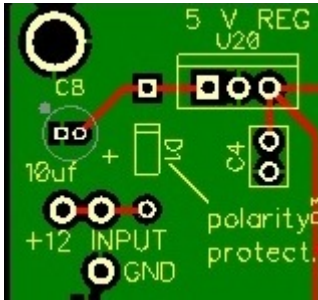

It is recommended that if you are going to use this option, build it first of all, so that you can check its output voltage accuracy -- it should be between 4.75-5.25 VDC. BEFORE POWERING, use an ohmmeter or very careful visual inspection to be sure you don't have a short on the input! The pins of the 10uF capacitor are very close, as are the pins of the voltage regulator and the output 0.1 uF capacitor and a short at any of these can have "undesired" impact. The first time you apply power, start LOW. As the input voltage rises above about 8V, the output should stabilize right at 5 V. The input diode if correctly installed, will protect you against accidental reverse voltage.

This option allows you to power the keyer from any source of 8-20VDC. The board includes a series 1-ampere diode, so if you connect the polarity backwards, it just won't power the board. Regulation down to 5VDC required by the Arduino is provided by a 3-terminal linear regular, LM7805, which includes thermal protection. Because the current requirements should be low (provided excessive LED back light current isn't chosen) no heatsink is necessary.

When installing the wire into the Power Pole connector, the crimp won't be solid unless you fold back several thickness of the small wire so that some grip is obtained. Even then, it may not be suitable and I recommend CAREFULLY soldering from the BACK entrance -- any solder on the tang of the pin will make it impossible seat properly in the red or black plastic holder. You will need to use a small screwdriver or other implement to push forward to "seat" the pin in the plastic holder. If you've never done that, you may want to get help.

REQUIRED PARTS

Input connectors - power pole	Wire for input connection (#18 or #20, red/black)	D1 - 1N4007 Be sure to install with the banded end of the diode on the banded end of the printed circuit board screenprint.
-------------------------------	---	--


<p>C8 10uF electrolytic Observe polarity when installing. The board is marked with + side, but many capacitors are only marked on the NEGATIVE side.</p>	<p>U20 5 Volt regulator Be certain that the metal tab is on the top side, as per the screen print.</p>	<p>C4 0.1 uF ceramic capacitor</p>
--	--	------------------------------------

Once the components have been installed, and SHORTS HAVE BEEN CORRECTED IF ANY, provide a voltage starting low as described above, and work your way up to 13.8VDC and test the output voltage.

THEORY OF OPERATION

The 7805 is a three terminal "linear" regulator that has an integrated circuit inside with some thermal and over current protection against shorts on the output. It can oscillate however, and for that reason input and output capacitors are used to reduce the feedback potentials from one end to the other of the device. If it is used for anything more than a few mA, it will need a small heatsink. The "05" at the end tells you it is for 5 volts. There are several other voltages available in the line of parts. There is also a "7905" that is intended to regulate NEGATIVE five volts, and a series there also.

PADDLE INPUT

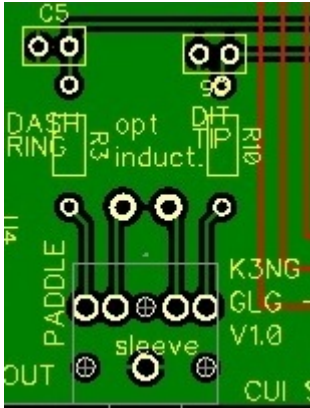

The paddle input brings the switch closures from the paddle to digital inputs D4 and D5. These inputs are biased "high" with internal resistors on the Arduino.

REQUIRED PARTS


<p>TRS Stereo 3.5mm jack for paddle input</p>	<p>Jumpers or inductors -- R3/R10 are place keepers for small inductors if you have severe problems with radio frequency interference. For now, install wire jumpers from cutoff portions of other computers or small sires.</p>	<p>0.01 uf bypass capacitors C5/C6. The markings on these capacitors are usually "103"</p>
---	--	--

Theory of Operation

Software sets internal "pull up" resistors on these inputs of the Arduino so that they see "high" when the paddles aren't pushed. The paddle consists of two switches that can short a wire to ground. When one or the other paddle is pressed, the input to the Arduino sees "low" as long as that voltage drops below some threshold, typically 0.8 VDC.

The capacitors on the lines are there to prevent interference from radio frequency pickup. If these aren't sufficient, then add some inductance (e.g. 1 uH) in series where provided. Keep the wires to the paddle close together which provides some inherent shielding protection. In really bad situations, use shielded cable for this wire, and connect the shield to ground.

KEYED LINE OUTPUT #1

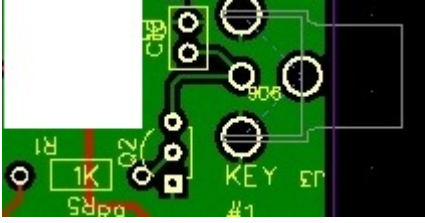

REQUIRED

This output allows the keyer to key positive-voltage keyed transceivers by grounding the key input with an open-collector output from a 2N3904. It cannot be used with negative voltage key lines, and certainly not with high negative voltage inputs like Heathkit vacuum tube transceivers from an earlier era -- use the reed relay output instead.


The maximum voltage and current that should be keyed are approximately +10VDC and 10 mA. Most transceivers will be well below this.

When the D7 output of the Arduino is driven high, 5 Volts begins to push current into the base of Q2 through the 1000 ohm resistor (approximately 4 mA; the Arduino may be able to push as much as 40mA but we don't want to overload it!). For normal keyed currents, this drives the transistor into full "saturation" and the collector voltage should be approximately 0.2 V, properly keying most transceivers

PARTS REQUIRED

RCA phono plug output connector J3	0.1 uf bypass capacitor	Q2 2N3904 transistor Be sure to install this with the flat end as shown on the screenprint. Avoid overheating the transistor. Maintain leads of about 2-4 mm between the transistor and the board, which will help with temperature protection.
R1 1000 ohms		


ARDUINO NANO

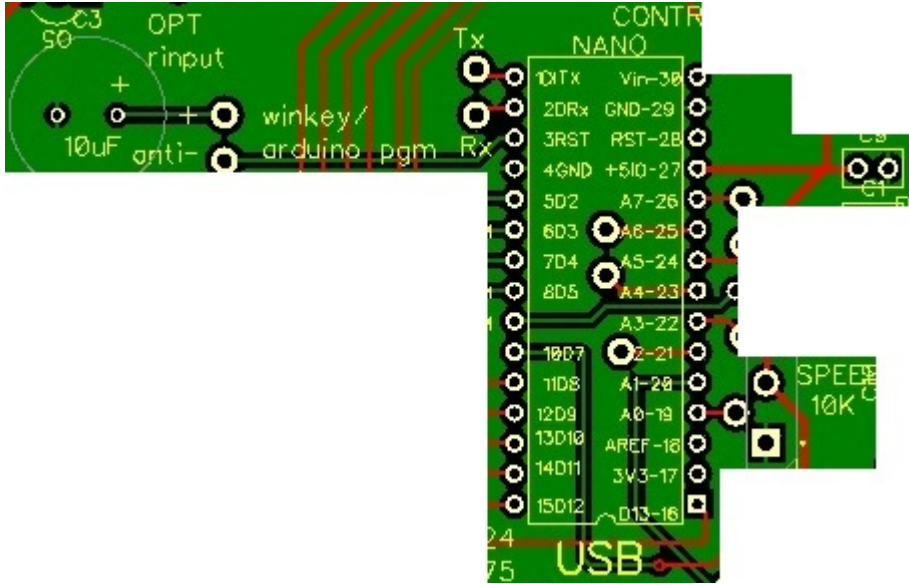

This part has 32 closely spaced pins. If yours comes without header pins, you'll need to solder the header pins to the Arduino and then the Arduino to the printed circuit board. You might want to use small spacers so the Arduino has a gap underneath it. That would make it easier to remove should you ever have to. Move quickly with the soldering iron to avoid overheating, and use just the required amount of thin rosin core solder to make a good connection. Don't leave a blob and be wary of any solder bridges. Use solder-wick to remove any bridges. Be certain the USB port is "down" as shown on the printed circuit board, and not "up"-

ARDUINO NANO		C9 0.1 uF bypass capacitor
<p>C3 10uF anti-reset capacitor</p> <p>Once the Arduino is verified to work, this is connected in and prevents the Arduino from be auto-reset each time a command is sent to it over the serial port.</p>	<p>Wires or switch to chose whether programming reset is allowed -- we are going to per-program our Arduinos and just use a jumper wire here with a small loop so we could cut it if needed to reprogram.</p>	<p>10K Speed potentiometer (panel mounted potentiometer) This may be marked 103</p>

OPTIONAL SPEAKER OUTPUT

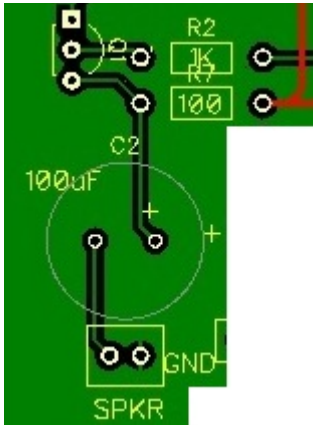


The speaker output is a square wave from the Arduino, amplified by transistor Q1 and AC-coupled to a small speaker by 100 uF capacitor C2. Be certain to observe polarity for C2.

The intensity of the volume is controlled by the choice of the value for R7. For loudest, pick 100 ohms. For fairly faint, pick 470 ohms.

<p>Speaker - any small speaker. 8 ohms nominal impedance, but will work with almost anything.</p> <p>You can double-stick-tape this to the bottom of your box or plywood base</p>	<p>C2 100 uF</p>	<p>Q1 2N3904 Be careful to observe the placement of the flat side of the transistor.</p>
<p>C8 10uF electrolytic Observe polarity when installing</p>	<p>U20 5 Volt regulator Be certain that the metal tab is on the top side, as per the screen print.</p>	<p>C4 0.1 uF ceramic capacitor</p>
<p>R2 1000 ohms BROWN BLACK RED</p>	<p>R7 -- choose value based on sound intensity requested, from 1000 ohms (very faint) to 100 ohms (loudest) 100 OHMS = BWN BLK BWN</p>	<p>Output terminals. If you prefer, you can put 0.1" header terminals here or otherwise just solder small wires to the speaker.</p>

--	--	--

2x16 Character LCD Display

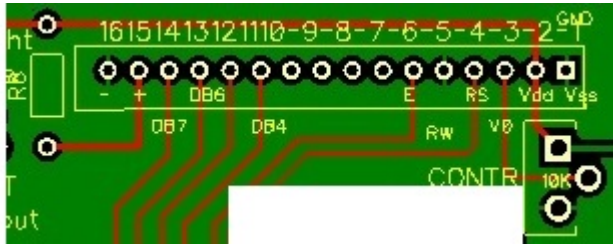

OPTIONAL


The LCD display must not be installed until AFTER the Arduino Nano, the contrast trimmer, 10uF C3, and portions of optional additional relay output (if installed) are soldered in, because they will be difficult to reach after the LCD is installed.

Be certain to recognize that the design places the display on the BACK side of the board, not on the Arduino side! Also be sure to use small spacer objects to keep the display off the board by 1/4" or more, so that it doesn't short out anything below it.

This is a standard inexpensive LCD alphanumeric display. For simplicity, in this design it is connected for 4bit (nibble) data. An alternative design might be to control it using I2C, but this was not chosen for this design. The display includes a backlight LED system, which must be fed a modest amount of current using dropping resistor R6 just to the left of the display. That resistor can be 470 ohms for modest lighting, all the way to 100 ohms for brighter.

LCD display	Screen brightness resistor 100 = bright 470 = moderate to dim
Contrast trimmer (10K)	

OPTIONAL PTT Radio Control

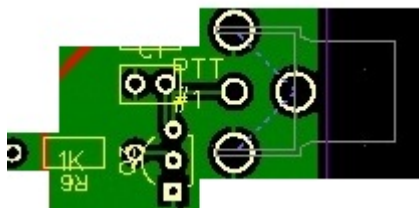

This isn't necessary, but it can be helpful for really fast paced contest contacts, because it can allow you to "un-transmit" faster than waiting for the VOX delay to expire when the last letter is transmitted. So I always use it in contests.

RCA Phono PTT output connector	Q3 2N3904 Transistor	C1 0.1 uf Capacitor
R6 1K resistor BROWN BLACK RED		

Theory of Operation

When the Arduino output goes high, it drives current through the 1K ohm resistor into the base of the transistor, pushing the transistor into full conduction (called "saturated"). Most transceivers provide a small positive voltage on their input and shorting this to ground with the saturated collector will push the radio into "transmit" mode. The normal delay going back to "receive" may be eliminated when this transistor goes quickly into non-conduction.

BE CAREFUL WITH OLDER TRANSCEIVERS -- Vacuum tube radios frequently used very large **NEGATIVE** voltages on these connections for push to talk, and that will destroy circuitry on this board! Use a relay output instead of a transistor output if you need to control push to talk on a vacuum tube older radio. Check that your radio does not source more than single digit milliamperes through its push to talk.

SPEED POTENTIOMETER

Very useful -- much much faster than working through menus.

10K potentiometer, connected by wires to the board.

The ones I normally use require a 0.375 (3/8") hole and a second hole for the indexing pin.

BUTTONS

10K resistor from +5 gets shorted to ground by Command button.

CAUTION: This MUST be 10K: BROWN BLACK ORANGE

1 K ohm resistor from the 10K goes to the Memory #1 button, which can short to ground

1 K ohm resistor next goes to the Memory #2 button, the other side of which is also connected to ground.

1 K ohm resistor goes to the Memory 3 button, and then a 1 K resistor from there to ground.

So a total of FOUR 1K resistors. These are BROWN BLACK RED.

Depending on which button shorts to ground, a different voltage shows up at the bottom of the 10K. It is zero when the command button is pushed, slightly greater when Memory #1 is pushed, again greater if Memory 2 is pushed and so on.

The buttons can be positioned pretty much anywhere, but the side of the box works well.

OPTIONAL RELAY KEY LINE OUTPUT



The optional relay keyed line output is as laid out, connected to "key output #2". Our software doesn't normally send to this output, so Resistor R4 can instead be diverted so that its top side comes from the Arduino output that feeds Key Line #1, allowing both open collector and the relay system to be keyed simultaneously. Otherwise, arrange for special programming of your unit to allow access to Key output #2.

There is an error in this portion of the board. Diode D2 is drawn with the cathode to the right, when it should be to the left.

Install the components including the transistor, diode, resistor and the 4 pin reed relay. The relay can go either way, but pin #1 is the square pin if you want to be exact; the part is symmetrical so it doesn't matter. Also add C7 the bypass capacitor and the phono socket output.

CODING NOTES

Subroutine

```
void command_mode()
```

Commands Implemented from CW at the paddle:

N - reverse paddles

O - cycle through side tone modes (off, paddles only, etc)

P - program memories (next digit is the number of the memory you program; then send text and end with closing command mode by pressing command button again)

T - set tuning mode

Y - set repeat delay [applies to all memory once turned on]

Unknown command - implemented (sends ?)

Commands at the paddle not implemented

A - iambic mode (default, not implemented)Un

B - B iambic mode (command not implemented)

C - single paddle mode (command not implemented)

E - announce speed (command not implemented)

D - Ultimatic mode (command not implemented)

G - bug mode (command not implemented)

H - weighting adjust (command not implemented)

I - toggle transmit (command not implemented)

J - adjust dit to dah (command not implemented)

L - weighting adjust (command not implemented)

M - command mode speed (set to 10) (command not implemented)

Q - set keying compensation (command not implemented)

R - set serial number (command not implemented)


V - toggle speed pot active (command not implemented)

W - change speed (command not implemented) (use speed potentiometer)

Code uses 96% of available program space

61% of available RAM

SCHEMATIC

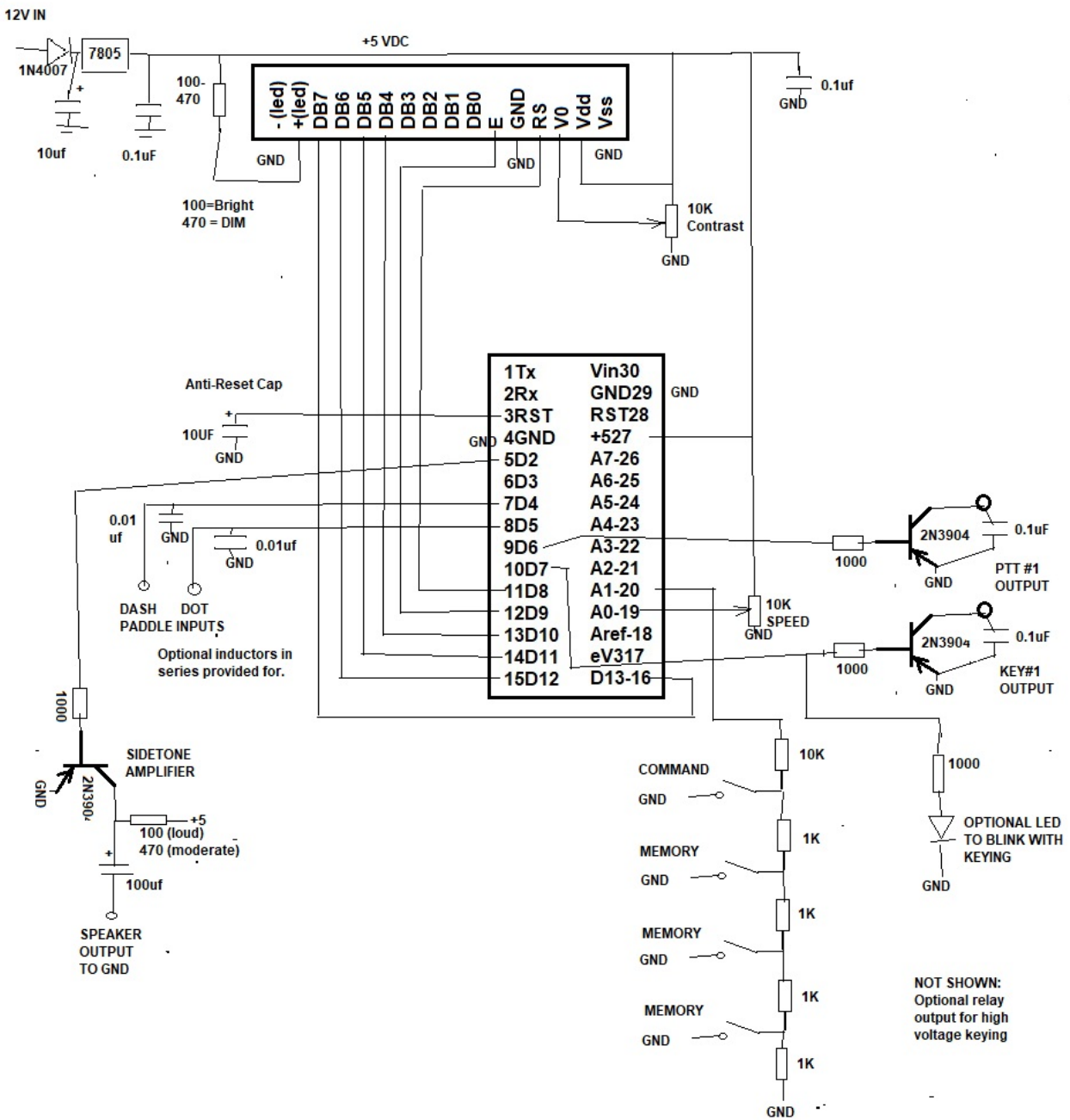

COMPONENTS REQUIRED

No.	Item	Quantity (max)	Comment
1	Arduino Nano	1	
2	2x16 LCD display	1	
3	RCA phono jacks	3	minimum 1, maximum 3
4	TRS stereo paddle jack	1	
5	10K trimmer potentiometer	1	contrast
6	10K panel potentiometer	1	speed (Req 0.375 drilled hole)
7	Momentary contact pushbutton	4	
8	Power Pole	1 pair	
9	7805 voltage regulator	1	optional
10	5V reed relay	1	OPTIONAL
11	2N3904 transistor	4	2 are optional
12	Diode	2	one for 12V power, 1 for reed relay
13	LED	1	optional; use 1K dropping resistor
14	1 K resistor	8	some optional with buttons
15	0.1 uf Capacitor ceramic	5	
16	0.01 uf capacitor	2	paddle terminals
17	10 uF electrolytic capacitor	2	no-reset, and 12V power input (opt)
18	100-500 ohm LED resistor	2	speaker and back light
19	100 uf capacitor	1	for speaker output; optional
20	small speaker	1	optional
21	10K resistor for button	1	top resistor
22	Plastic box	1	
23	Standoffs	4	
24	3mm screws/nuts	4ea	
25	16 pin header	1	

APPROXIMATE COST, AUGUST 2024

Select	INCLUDES	CAPABILITIES	INCRE-MENTAL CHARGE
<input type="checkbox"/>	<ul style="list-style-type: none"> • BASE unit mounted open on wood • Printed circuit board • Arduino Nano (https://www.amazon.com/gp/product/B07G99NNXL) • Key & PTT 2N3904 outputs • USB short cable to Nano • One command button • Speed Potentiometer • No Display • No Box (case) • No Relay output <p>YOU provide tiny speaker (e.g. from Baofeng mic)</p> <p>YOU provide paddle system with TRS 3.5 mm stereo plug to connect to provided TRS 3.5 mm JACK on printed circuit board.</p>	<ul style="list-style-type: none"> • Fully functional iambic keyer with TRS stereo jack for paddle input • Speed adjustable from 10-30 wpm • Command speed set to 10 wpm • Capable of keying most modern solid state transceivers via its open-collector 2N3904 outputs (~up to 10V, 20mA) • Can control push-to-talk also • (Build your keying cable from stereo cable and either 1/4" or 1/8" plug as needed for your radio, not included here.) • Fully functional WINKEYER connection to N3FJP (tested) and likely most other modern logging systems. • Keying speed controlled primarily via Potentiometer, but can also be controlled by paddle (hold command key down, press left paddle to speed up, right paddle to slow down) 	<p>Board \$5.33 Connectors \$6.00 Transistors \$0.60 Resistors \$0.60 Electrolytics \$0.50 Ceramics \$0.50 Button \$0.53 Arduino Nano \$5.00 4 standoffs \$0.56</p> <p>TOTAL \$20.72</p>
<input type="checkbox"/>	<ul style="list-style-type: none"> • Add Small speaker 	<ul style="list-style-type: none"> • (Option provided in case you don't have one) -- you are likely to want the side tone • Something similar to this: • https://www.amazon.com/Metal-Shell-Internal-Magnet-Speaker/dp/B0B5KZL868 	Adds \$1.25
<input type="checkbox"/>	<ul style="list-style-type: none"> • Add three buttons for Memories • Add required Resistors for buttons 	<ul style="list-style-type: none"> • Allows up to three canned texts to be programmed and/or initiated, and each can be individually set to "repeat"; the repeat time can be set (but not 	Adds \$2

		individually)	
<input type="checkbox"/>	<ul style="list-style-type: none"> Add plastic box 	<ul style="list-style-type: none"> Nice box from Amazon Drill points copied from my prototype https://www.amazon.com/Raculety-Waterproof-Electrical-Electronic-Enclosure/dp/B089K1KBL6 	Adds \$7.50 plus you get the experience of DRILLING
<input type="checkbox"/>	<ul style="list-style-type: none"> Add 2-line LCD display and header and trimmer potentiometer 	<ul style="list-style-type: none"> The display shows the speed when you change it, and always shows the code being transmitted as well. Makes programming memories a little more obvious also. Example: https://www.amazon.com/gp/product/B00HJ6AFW6 Header from stock -- https://www.amazon.com/gp/product/B09G5RF3H6 	Adds \$5.00 plus you get the experience of DRILLING and SAWING
<input type="checkbox"/>	<ul style="list-style-type: none"> Add reed-relay output for radios with negative or high voltage keying voltage (e.g. Heathkits) 	<ul style="list-style-type: none"> Relay similar to https://www.amazon.com/HiLetgo-SIP-1A05-Switch-Resistance-450-550ohm/dp/B09KGYWPP plus 2N3904 and a few small components 	Adds \$3
<input type="checkbox"/>	<ul style="list-style-type: none"> Add little LED to flash when keying 	<ul style="list-style-type: none"> Just so you can see it if you want. 	Adds \$0.50
<input type="checkbox"/>	<ul style="list-style-type: none"> Add 12V input power option with three terminal regular and power pole connector assembly 	<ul style="list-style-type: none"> Allows keyer to operate from 12V without need for any computer L7805 regulator, a few capacitors, and power pole https://www.amazon.com/outstanding-L7805CV-Regulator-Positive-Three-Terminal/dp/B08HGDG6WB 	Adds \$4 and you get the experience of crimping power poles (use multiple folded of small wires to be sure it crimps properly)

		<ul style="list-style-type: none"> • Genuine Anderson power pole connectors: • https://www.amazon.com/Anderson-PP15-12-16-AWG-Set/dp/B07BKSXF4G 	
	You add up the total for all the options YOU would like:		TOTAL